

① Les signaux sont alternatifs sinusoidaux.

$$I_{\max} = 3 \text{ dir} \times 1 \text{ A/dir}$$

$$V_{\max} = 3 \text{ dir} \times 1 \text{ V/dir}$$

$$I = \frac{I_{\max}}{\sqrt{2}}$$

$$I = 2,13 \text{ A}$$

$$I_{\max} = 3 \text{ A}$$

$$V_{\max} = 3 \text{ V}$$

$$V_{\max} = \frac{V}{2}$$

$$V_{\max} = 2,13 \text{ V}$$

$$T = 6,2 \text{ dir} \times 1 \text{ ms/dir}$$

$$T = 6,2 \text{ ms}$$

$$f = \frac{1}{T}$$

$$f = \frac{1}{0,0062}$$

$$f = 161 \text{ Hz}$$

$$\omega = 2\pi f$$

$$\omega = 1010 \text{ rad.s}^{-1}$$

$$\Delta t = +1,6 \text{ dir} \times 1 \text{ ms/dir} \quad \underline{\Delta t = 1,6 \text{ ms}}$$

$$\varphi = \frac{2\pi}{T} \cdot \Delta t$$

$$\varphi = \frac{2\pi}{0,0062} \cdot 0,0016$$

$$\varphi = 1,62 \text{ rad} \\ \xrightarrow{\frac{180^\circ}{\pi}} 93^\circ$$

(sensiblement en quadrature)

⑤ La tension est en avance de la courant.

$$i(t) = \sqrt{2} I \sin(\omega t)$$

$$i(t) = 3 \sin(1000t)$$

$$u(t) = \sqrt{2} V \sin(\omega t + \varphi)$$

$$u(t) = 3 \sin(1000t + 1,82)$$

$$\langle i \rangle = \frac{1}{T} \int_0^T \sqrt{2} I \sin(\omega t) dt = \frac{1}{2\pi} \int_0^{2\pi} \sqrt{2} I \sin(\theta) d\theta$$

$$\langle i \rangle = \frac{1}{2\pi} \left[-\sqrt{2} I \cos(\theta) \right]_0^{2\pi} = \frac{1}{2\pi} \left(-\sqrt{2} I \underset{=1}{\cancel{\cos(2\pi)}} - (-\sqrt{2} I \underset{=1}{\cancel{\cos(0)}}) \right)$$

$$\langle i \rangle = 0$$

⑧ Aucun changement sur le chronogramme car la composante continue de $i(t)$ et $v(t)$ est nulle.

⑨ Le signal $v(t)$ est continu car $v(t) \geq 0$.

$$\underline{v_{\max} = 20 \text{ V}} \\ \underline{T = 0,003 \text{ s}}$$

$$f = \frac{1}{T}$$

$$f = \frac{1}{0,003}$$

$$f = 333 \text{ Hz}$$

$$\text{⑩ } t \in [0; \frac{T}{3}] : v(t) = V_{\max}$$

$$t \in [\frac{T}{3}; T] : v(t) = 0$$

$$\text{⑪ } \langle v \rangle = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \left(\int_0^{T/3} V_{\max} dt + \int_{T/3}^T 0 dt \right)$$

$$\langle v \rangle = \frac{1}{T} \left[V_{\max} t \right]_0^{T/3} \xrightarrow{T/3} \text{aire sous la courbe} \rightarrow 0$$

$$\langle v \rangle = \frac{1}{T} V_{\max} \frac{T}{3}$$

$$\langle v \rangle = \frac{V_{\max}}{3} \quad \underline{\langle v \rangle = 6,67 \text{ V}}$$

$$\text{⑫ } V = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} = \sqrt{\frac{1}{T} \left(\int_0^{T/3} V_{\max}^2 dt + \int_{T/3}^T 0 \cdot dt \right)}$$

$$V = \sqrt{\frac{1}{T} \left[V_{\max}^2 t \right]_0^{T/3}} = \sqrt{\frac{1}{T} V_{\max}^2 \frac{T}{3}} = 0$$

$$V = \frac{V_{\max}}{\sqrt{3}}$$

$$V = \frac{20}{\sqrt{3}} \quad \underline{V = 11,5 \text{ V}}$$

$$\text{⑬ } P_N = \langle v \rangle \cdot I \quad P_N = 11,5 \times 5 \quad \underline{P_N = 57,5 \text{ W}}$$

$$\text{⑭ } P_J = R I^2 \quad P_J = \frac{V^2}{R} \quad P_J = \frac{11,5^2}{100} \quad \underline{P_J = 1,32 \text{ W}}$$

$$\textcircled{16} \text{ Loi des noeuds : } i_R(t) + i(t) = I_0 \quad (1)$$

$$\text{Loi des mailles : } u_R(t) = u_C(t) \quad (2)$$

Caractéristiques :

$$\text{condensateur : } i(t) = C \frac{du_C}{dt} \quad (3)$$

$$\text{résistance : } u_R(t) = R \cdot i_R(t) \xrightarrow{(2)} i_R(t) = \frac{u_C(t)}{R}$$

$$\text{Finalement } \frac{u_C(t)}{R} + C \frac{du_C}{dt}(t) = I_0$$

$$u_C(t) + \underbrace{RC \frac{du_C}{dt}(t)}_{\zeta = RC} = R I_0$$

$$\textcircled{17} \text{ Solution homogène } k e^{-t/\zeta} \quad \left. \begin{array}{l} \\ R I_0 \end{array} \right\} \quad u_C(t) = R I_0 + k e^{-t/\zeta}$$

$$\text{Condition initiale } u_C(0) = 0 \Rightarrow 0 = R I_0 + k e^0 \Rightarrow k = -R I_0$$

$$\text{Finalement } \boxed{u_C(t) = R I_0 (1 - e^{-t/RC})}$$